

Question number: 1

Resistor : 4Ω

Resistor : 2Ω

High source - $8V$

Solve :-

$$R_{eq} = 4 + 2 = 6\Omega$$

$$32 - 4I - 8 - 2I = 0$$

$$24 - 6I = 0$$

$$I = 4A$$

$$V_1 = 4\Omega \times 4A = 16V$$

$$V_2 = 2\Omega \times 4A = 8V$$

$$= V_1 = 16V, V_2 = 8V$$

TUESDAY 27
22 صفر

Evening

Question 2

10 Ω resistor $\rightarrow V_u$

5 Ω resistor $\rightarrow V_o$

Source = 70V

Dependent source = $2V_u$

Loop current I

$$V_u = 10I$$

$$V_o = 5I$$

Evening

KVL

$$70 - 10I - 2V_u - 5I = 0$$

$$70 - 35I = 0$$

24 SATURDAY
19 صفر

25 SUNDAY
20 صفر

$$I = 2A$$

$$V_u = 10 \times 2 = 20V$$

$$V_o = 5 \times 2 = 10V$$

$$V_u = 20V, V_o = 10V$$

09

Question 3

10

$$10\Omega + 6\Omega = 16\Omega$$

11

12

$$R = \frac{12 \times 16}{12 + 16} = \frac{192}{28} = 6.86\Omega$$

01

02

03

$$6.86 + 8 = 14.86\Omega$$

04

$$R = \frac{6 \times 14.86}{6 + 14.86} = 4.27\Omega$$

05

Evening

$$4 + 4.27 = 8.27\Omega$$

$$3\Omega$$

29 THURSDAY
24 صفر

$$R_{eq} = 8.27 + 3 = 11.27\Omega$$

09

10

$$R_{eq} = 11.27\Omega$$

11

12

01

Question 4

$$50 \mu F + 70 \mu F = 120 \mu F$$

$$\frac{1}{C} = \frac{1}{60} + \frac{1}{20}$$

$$C = 40 \mu F$$

$$40 + 20 = 60 \mu F$$

$$\frac{1}{C_{eq}} = \frac{1}{20} + \frac{1}{60}$$

$$C_{eq} = 40 \mu F$$

SUNDAY 1 27 صفر SATURDAY 31 26 صفر

Question 5 -

$$C_{eq} = 20 + 30 = 50 \mu F$$

$$Q = C_{eq} \times V = 50 \times 150 = 7500 \mu C$$

$$V_1 = \frac{Q}{40} = 187.5 V$$

$$V_3 = \frac{Q}{60} = 125 V$$

$$V_2 = \frac{Q}{20} = 375 V$$

$$V_4 = \frac{Q}{30} = 250 V$$

3 TUESDAY
29 صفر

$$V_1 = 187.5 V, V_2 = 375 V$$

$$V_3 = 125 V, V_4 = 250 V$$

Question 6

$$4 + 20 = 24H$$

$$8 + 10 = 18H$$

$$I_{eq} = 24 + 2 + 12 + 18$$

$$I_{eq} = 61H$$

Question 7

$$\frac{1}{L} = \frac{1}{50} + \frac{1}{40} + \frac{1}{30} + \frac{1}{20}$$

THURSDAY 5
1 ربيع الاول

$$20 + 100 + 40 = 160. mA$$

$$I_{eq} = 167.3 mA$$

$$I_{eq} = 167.3 mA$$

Evening